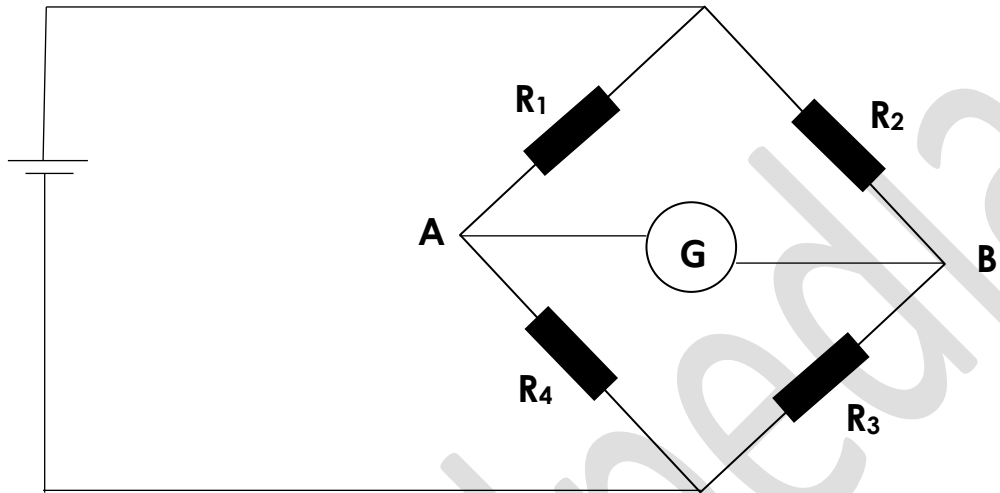


Wheatstone Bridge



If ,

$$\frac{R_1}{R_4} = \frac{R_2}{R_3}$$

Galvanometer will not be deflected.

AS $V_A = V_B$.

- **Direction**

Go to Current Electricity → Easy patterns to learn more about these bridges.