Resistors

• Electrical resistance

$$R = (\rho I)/A$$

R = Resistance

 ρ = Resistivity

A = Cross sectional area

I = The length of the conductor

- Resistance (ρ) = RA/I
- Conductance (G) = 1/G
- Conductivity (σ) = $1/\rho$

• Changing of resistance with temperature

$$R_{\theta} = R_0(1 + \alpha \theta)$$

R₀₌ Resistance at 0 °C


a = Temperature Coefficient of Resistance

 θ = temperature of resistor

 R_{θ} =Value of resistance at the considered temperature

• Ohm rule

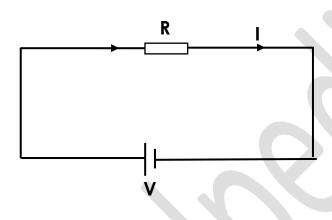➤ When physical factors such as the temperature of a conductor remain constant, the potential gap is inversely proportional to the current.



$$V = IR$$

Resistance systems


1. Series resistor systems

$$R_1$$
 R_2 => R

$$R = R_1 + R_2$$

- > The same current flows through series resistors.
- The sum of the potentials of resistors are equal to the potential of equatorial potential.

2. Parallel resistance systems

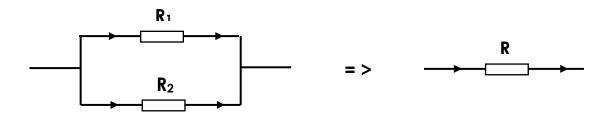

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

- Same potential difference to every resistor, but current will be divided.
- If resistance is high, the current is low.